## **CE/CZ3001: Advanced Computer Architecture**

## **Tutorial-3**

(Consider the datapath in Figure 1 to find the answers)

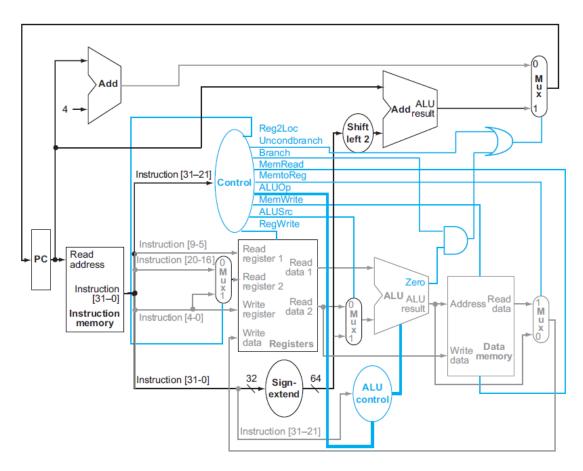


Figure 1: Datapath for R-format, I-format, D-format and B format: for ALU, load/store, conditional branch, and jump instructions.

- 1. Which types of instructions require the following hardware resources?
  - (i) PC increment circuit
  - (ii) instruction memory
  - (iii) register file
  - (iv) ALU
  - (v) data memory

## (Answer:

- (i) **PC increment circuit** is used for ALL instructions.
- (ii)  $\mbox{\bf Instruction memory}$  is used for ALL instructions.
- (iii) Register file is used for all instructions except 'unconditional branch'.
- (iv) ALU is used for R-type ALU instructions, immediate ALU instructions, load, store and conditional branch instructions.
- (v) **Data memory** is used for load and store instructions.

- 2. Based on the propagation delay provided in the Table 1, find the execution-time of the following instructions.
  - (i) R-format instructions
  - (ii) I- format instructions
  - (iii) load word (LDUR)
  - (iv) store word (STUR)
  - (v) conditional branch (CBZ)
  - (vi) unconditional branch (B)

Table 1: Propagation Delay of Different Hardware Elements in the Datapath

PC++	PCin→PCout	I-MEM (R)	ADD	MUX	REG (R/W)	ALU	D-MEM (R/W)	Sign- Extend	Shift- Left-2
800 ps	100 ps	500 ps	1500 ps	50 ps	200 ps	2000 ps	2000 ps	25 ps	0

Note: PC++ stands for the delay for PC increment, i.e., time required to add 4 with PC to compute PC+4. I-MEM (R) stands for the time for reading instruction memory, and D-MEM (R/W) stands for the time required for read or write operation on data memory. REG (R/W) stands for the time required for read or write operation on register file.

(Answer: (i) 3050, (ii) 2950, (iii) 4950, (iv) 4700, (vi) 2950, (vii) 2175)

- 3. Based on the propagation delays listed in Table 1.
  - (i) Find the duration of minimum clock period of single-cycle datapath.
  - (ii) If we implement the IF, ID, EX, MA, and WB in different clock cycles, then what would be the minimum duration of clock period?

(Answer: (i) 4950 ps, (ii) 2000 ps)